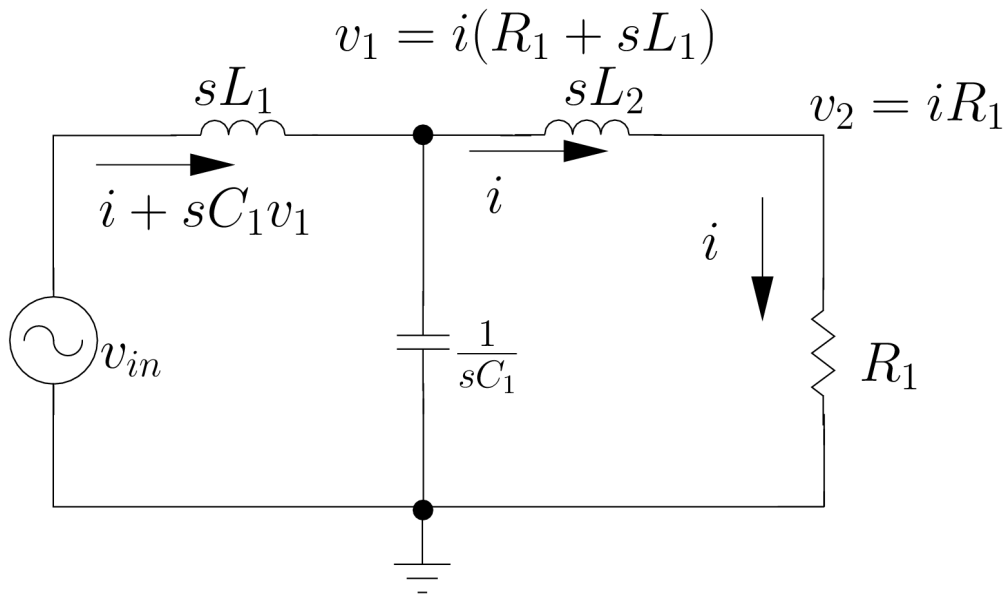


Circuit Analysis:



let us take the above circuit into consideration, with three nodes namely:

- v_{in}
- v_1
- v_2

and i is the current passing through them.

1. Considering node v_2 :

$$v_2 = iR_1 \tag{Equation 1}$$

2. Now at node v_1 :

$$v_1 = v_2 + isL_2 \tag{Equation 2}$$

$$v_1 = i(R_1 + sL_2) \tag{Equation 3}$$

3. To determine v_{in} :

$$v_{in} = sL_1\left(i + \frac{v_1}{\frac{1}{sC_1}}\right) + v_1 \tag{Equation 4}$$

$$v_{in} = sL_1\left(i + i(R_1 + sL_2)sC_1\right) + i(R_1 + sL_2) \tag{Equation 5}$$

$$v_{in} = i\left(sL_1(1 + sC_1R_1 + s^2C_1L_2) + R_1 + sL_2\right) \tag{Equation 6}$$

4. The current **i** can be obtained from the **equation 6** :

$$i = \frac{vin}{(sL_1 + s^2C_1R_1L_1 + s^3C_1L_1L_2 + R_1 + sL_2)} \quad (\text{Equation 7})$$

5. v_1 and v_2 in terms of vin :

$$v_2 = \frac{vinR_1}{(sL_1 + s^2C_1R_1L_1 + s^3C_1L_1L_2 + R_1 + sL_2)} \quad (\text{Equation 8})$$

$$v_1 = \frac{vin(R_1 + sL_2)}{(sL_1 + s^2C_1R_1L_1 + s^3C_1L_1L_2 + R_1 + sL_2)} \quad (\text{Equation 9})$$